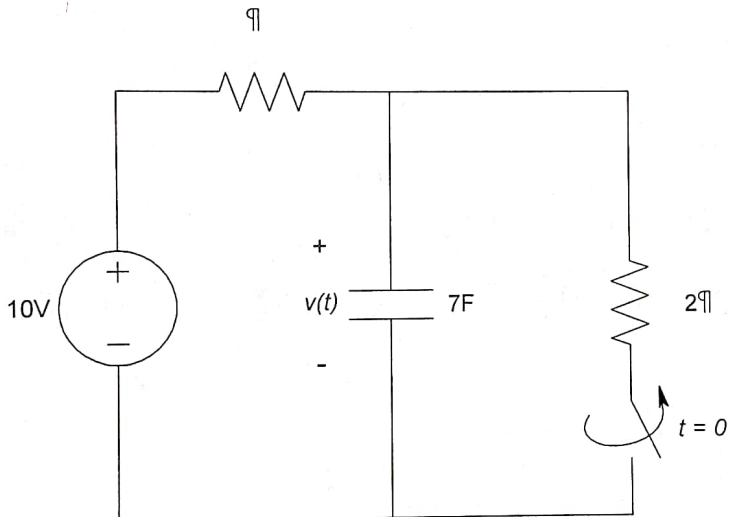


PART-A (15 Marks)

Q.No.-1. Answer the following questions carrying one mark each.


15

(i).	What is cutset matrix?
(ii).	Define singularity functions.
(iii).	In the circuit of Fig.1., the capacitor voltage just before $t = 0$ is _____:
 <p style="text-align: center;">Fig.1.</p>	
(iv).	Define the transient response of a circuit.
(v).	Define poles and zeros of a function.
(vi).	Explain the difference between driving point function and transfer function.
(vii).	List four different parameters of two port networks.
(viii).	Write the condition of reciprocity of a network in terms of h-parameters.
(ix).	Show [Z] parameters in terms of [Y] parameters.
(x).	What are the specifications of Low Pass and High Pass Filters?
(xi).	A constant k high pass p section has a characteristic impedance of 300Ω at $f = \infty$. At $f = f_c$, the characteristic impedance will be _____.
(xii).	An m derived low pass filter has $f_c = 1000 \text{ Hz}$ and $m = 0.6$. This filter will have infinite attenuation at $f_\infty =$ _____ Hz.
(xiii).	Discuss the demerits of m-derived Filters?
(xiv).	Define positive real functions.

(xv). Differentiate Foster Form and Cauer Form.

PART B (20 Marks)

Answer the following questions, one from each unit & all question carry equal marks. 5x4=20

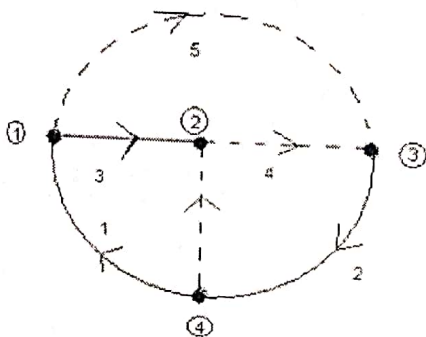UNIT-I		
2	For the tree shown in Fig.2, develop the fundamental cut-set matrix.	5
 <p style="text-align: center;">Fig.2.</p>		
UNIT-II		
3	Discuss various restrictions on pole and zero locations for driving point function	5
UNIT-III		
4	Determine the [Y] parameters of a two-port network whose Z parameters are	5
$[Z] = \begin{bmatrix} 10 & 4 \\ 4 & 10 \end{bmatrix} \Omega$		
UNIT-IV		
5	Define and explain positive real functions with its various properties.	5

PART-C (40 Marks)

Students are required to attempt four question, by selecting at least one question from each unit & all question carrying equal marks. 10x4=40

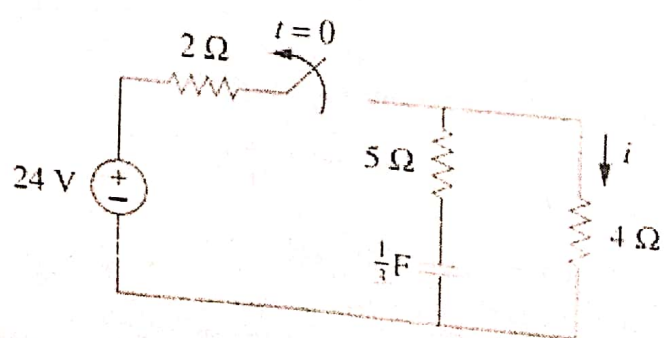
UNIT-I		
6	Derive and explain the Step Response of series RLC circuit.	10
7	For the circuit shown in Fig.3, find $i(t)$ for $t > 0$.	10
		

Fig.3.

UNIT-II

- 8 For the circuit shown in Fig.4, the switch is opened at $t=0$. Find the node voltages $v_1(t)$ & $v_2(t)$. 10
- $L = 0.5\text{h}$ $C = 1\text{f}$ $G = 1\text{ mho}$ $V = 1\text{v}$.

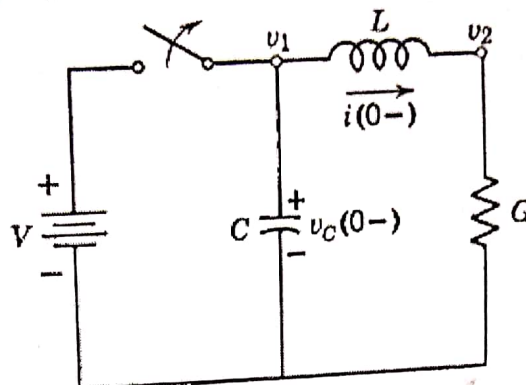


Fig.4.

- 9 Describe various restrictions on pole and zero locations for transfer functions. 10

UNIT-III

- 10 Determine the Z parameters for the two-port shown in Fig. 5. 10

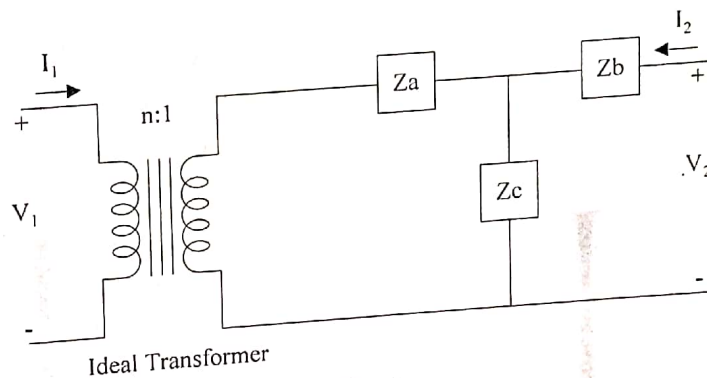


Fig.5.

- 11 Determine the ABCD parameters for the two-port shown in Fig. 6. 10

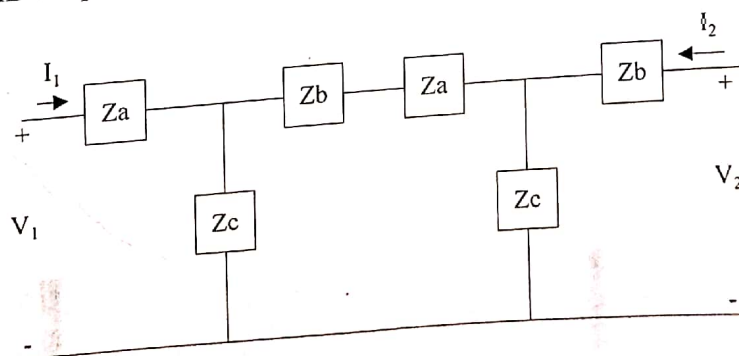


Fig. 6.

UNIT-IV

- 12 Design m-derived T-sections HPFs for $R_0 = 600\text{ ohms}$, $f_c = 1800\text{ Hz}$ and $f_\infty = 2000\text{ Hz}$. 10
- 13 An impedance is given by $Z(s) = \frac{3s^2 + 18s + 24}{s^2 + 3s}$. Realize the network in Cauer-I form. 10