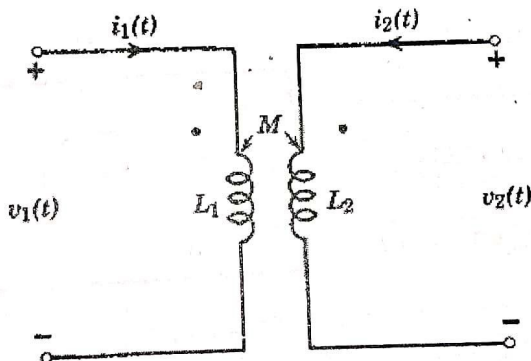


Note: All questions in Part-A and Part-B are compulsory. Attempt any four questions from Part-C selecting at least one from each unit.

PART-A (15 Marks)

Q.No.-1. Answer the following questions carrying one mark each.

15

(i).	What is incidence matrix?
(ii).	Define the concept of network analysis.
(iii).	In the circuit of Fig.1., draw the Laplace equivalent circuit.
 <p style="text-align: center;">Fig.1.</p>	
(iv).	Define the transient response of a circuit.
(v).	Define poles and zeros of a function.
(vi).	Explain the difference between driving point function and transfer function.
(vii).	List four different parameters of two port networks.
(viii).	Write the condition of symmetry of a network in terms of h-parameters.
(ix).	Show [Y] parameters in terms of [Z] parameters.
(x).	What are the specifications of m-derived Filters?
(xi).	A constant k high pass pi section has a characteristic impedance of 300 Ω at $f = \infty$. At $f = f_c$, the characteristic impedance will be _____.
(xii).	An m derived low pass filter has $f_c = 1000$ Hz and $m = 0.4$. This filter will have infinite attenuation at $f_\infty =$ _____ Hz.
(xiii).	Discuss the demerits of constant-k filters?

(xiv).	Define positive real functions.
(xv).	Differentiate Foster Form and Cauer Form.

PART B (20 Marks)

UNIT-I		5
2	For the tree shown in Fig.2, develop the fundamental cut-set matrix.	

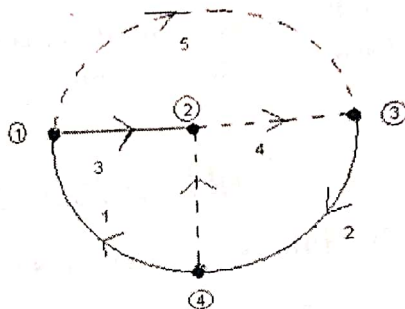


Fig.2.

UNIT-II		5
3	For the circuit shown in Fig.3, find impulse response of the current $i(t)$ using Laplace Transform.	

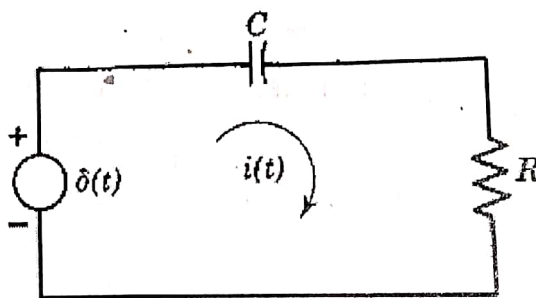


Fig.3

UNIT-III		5
4	Determine the $[Z]$ parameters of a two-port network whose Y parameters are	

$$[Y] = \begin{bmatrix} 10 & 4 \\ 4 & 10 \end{bmatrix} \Omega$$

UNIT-IV		5
5	Define and explain positive real functions with its various properties.	

PART-C (40 Marks)

UNIT-I		
6	Derive and explain the Step Response of parallel RLC circuit.	10
7	For the circuit shown in Fig.4, find $i_1(0+)$, $i_2(0+)$ and $i_1(\infty)$.	1

3(3)

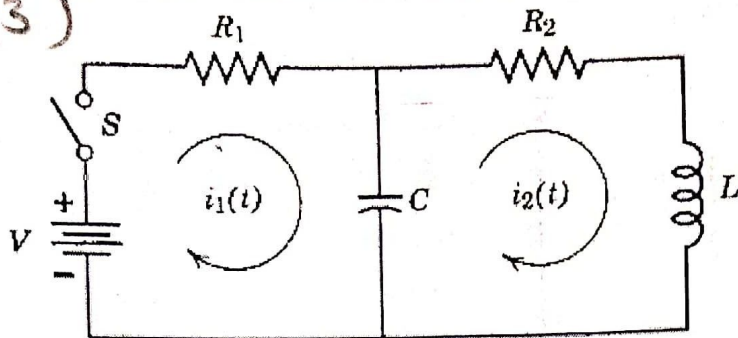


Fig.4.

UNIT-II

- 8 For the circuit shown in Fig.5, the switch is thrown from position 1 to 2 at $t=0$. Just before the switch is thrown, the initial conditions are $i_L(0^-) = 2A$ and $v_C(0^-) = 2V$. Find the current $i_1(t)$ after the switching action using Laplace Transform.

10

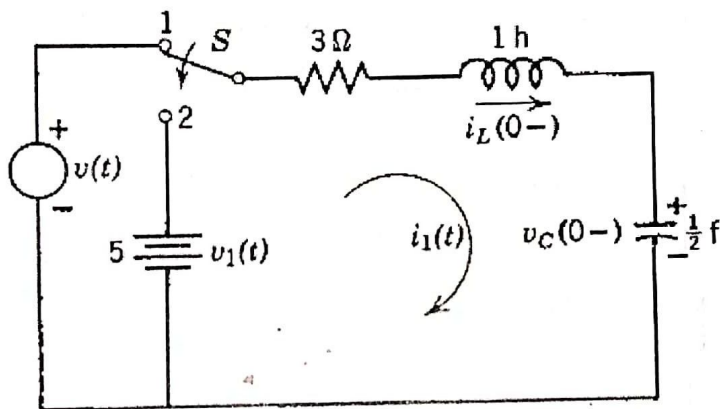


Fig.5.

- 9 Describe various restrictions on pole and zero locations for transfer functions.

10

UNIT-III

- 10 Determine the ABCD parameters for the two-port shown in Fig. 6.

10

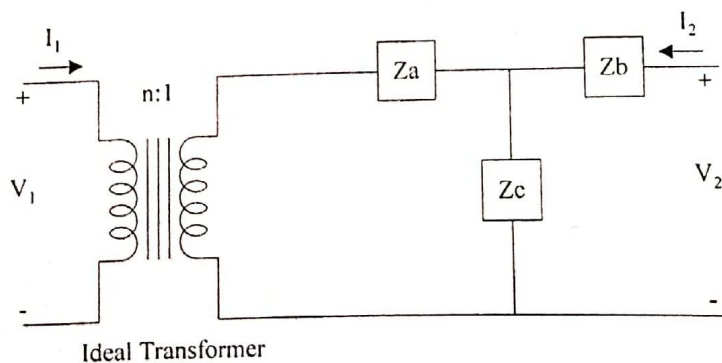


Fig.6.

- 11 Determine the Z parameters for the two-port shown in Fig. 7.

10

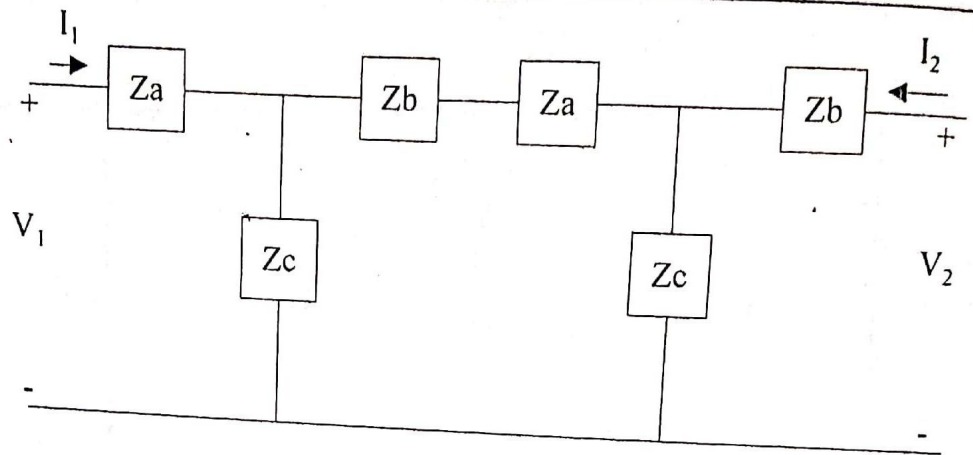


Fig. 7.

UNIT-IV

12	Design m-derived π -section LPF for $R_0 = 600$ ohms, $f_c = 1800$ Hz and $f_\infty = 2000$ Hz.	10
13	An impedance is given by $Z(s) = \frac{2s^5 + 12s^3 + 16s}{s^4 + 4s^2 + 3}$ Realize the network in Cauer-I form.	10