

THEORY EXAMINATION – DECEMBER 2019

TIME- 3 HRS

B. Tech (Electronics & Communication Engineering) 3rd Semester

M.M. -75

COURSE NO.: EC-213


COURSE TITLE: Network Theory

PART-A (15 Marks)

1. Answer the following multiple-choice questions.

15

1	What is incidence matrix?
2	In an electric circuit, the dual of resistance is: (a) conductance (b) inductance (c) capacitance (d) open circuit
3	If v_x changes from 2 V to 4 V at $t = 0$, we may express v_x as: (a) $\delta(t)$ V (b) $2u(t)$ V (c) $2u(-t) + 4u(t)$ V (d) $4u(t) - 2$ V
4	Define the transient response of a circuit.
5	If the input to a linear system is $\delta(t)$ and the output is $e^{-2t}u(t)$, the transfer function of the system is: (a) $\frac{1}{s+2}$ (b) $\frac{1}{s-2}$ (c) $\frac{s}{s+2}$ (d) $\frac{s}{s-2}$ $1 + \frac{s}{s+2} \quad s + \frac{2+1}{s+2}$
6	A zero of the transfer function $H(s) = \frac{10(s+1)}{(s+2)(s+3)}$ is at (a) 10 (b) -1 (c) -2 (d) -3
7	The impedance of a 10-F capacitor is: (a) $10/s$ (b) $s/10$ (c) $1/10s$ (d) $10s$
8	In the circuit of Fig.1., draw the Laplace equivalent circuit.

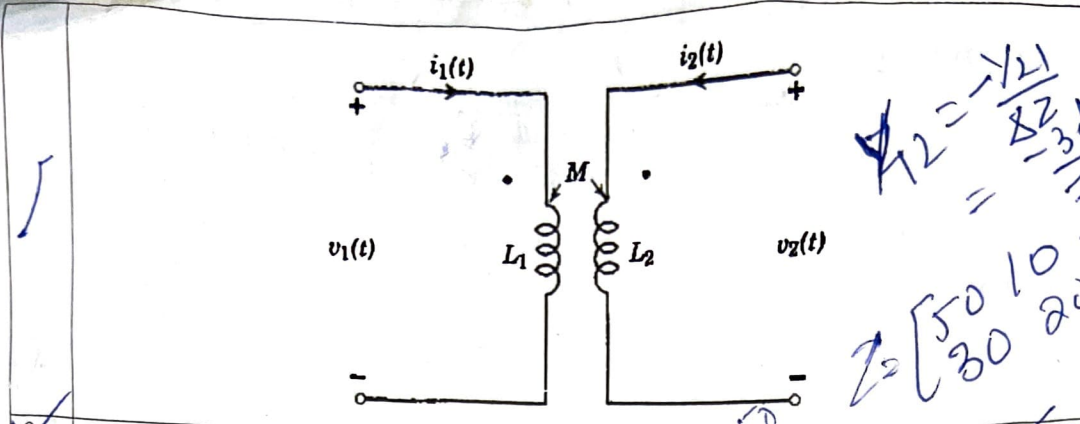

Handwritten calculations:

$$V_{12} = \frac{-121}{82} = -\frac{39}{20} \phi$$

$$Z = \begin{bmatrix} 50 & 10 \\ 30 & 20 \end{bmatrix}$$

$$Z = \begin{bmatrix} 20 & -10 \\ -30 & 50 \end{bmatrix}$$

$$Z_{11} = 50$$

$$Z_{22} =$$

- 9 A two-port is described by the following equations:
- $$V_1 = 50I_1 + 10I_2$$
- $$V_2 = 30I_1 + 20I_2$$
- Which of the following is *not* true?
- (a) $z_{12} = 10$ (b) $y_{12} = -0.0143$
 (c) $h_{12} = 0.5$ (d) $A = 50$
- 10 If a two-port is reciprocal, which of the following is *not* true?
- (a) $z_{21} = z_{12}$ (b) $y_{21} = y_{12}$
 (c) $h_{21} = h_{12}$ (d) $AD = BC + 1$
- 11 What are the specifications of Low Pass and High Pass Filters?
- 12 An m derived low pass filter has $f_c = 2000$ Hz and $m = 0.3$. This filter will have infinite attenuation at $f_\infty =$ _____ Hz.
- 13 List the demerits of constant-k filters?
- 14 Define positive real functions.
- 15 List various properties of R-C impedance functions.

PART B (20 Marks)

Answer the following questions, one from each unit & all question carrying equal marks.

UNIT-I		5x4=20
2	Derive and explain the Step Response of RC circuit.	5
UNIT-II		
3	Determine the transfer function $H(s) = \frac{V_o(s)}{I_o(s)}$ of the circuit as shown in Fig. 2.	5


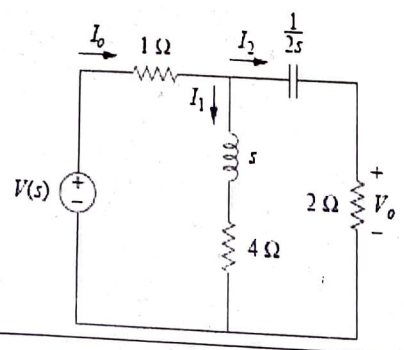
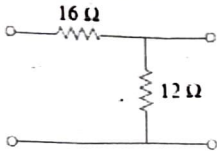
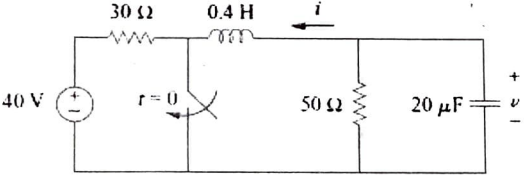
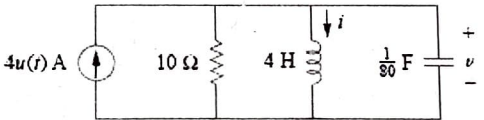
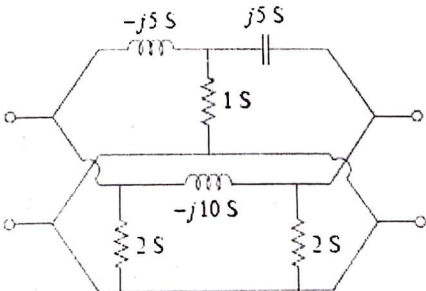


Fig 2		
UNIT-III		
4	Determine the Z parameters of the circuit as shown in Fig. 3.	5
		
Fig 3		
UNIT-IV		
5	Explain the concept of causality & stability in network synthesis.	5

PART-C (40 Marks)

Students are required to attempt four question, by selecting at least one question from each unit & all question carrying equal marks. 10x4=40

UNIT-I		
6	Derive and explain the step response of parallel RLC circuit.	10
7	Find $v(t)$ for $t > 0$ in the RLC circuit of Fig.	10
		
UNIT-II		
8	Consider the parallel RLC circuit. Using Laplace Transform, find $v(t)$ and $i(t)$ given that $v(0)=5V$ and $i(0)=-2A$.	10
		
9	Describe various restrictions on pole-zero locations for transfer functions.	10
UNIT-III		
10	Determine the Y parameters for the two-port shown in Fig.	10
		
11	Determine the ABCD parameters for the two-port shown in Fig.	10
<p style="text-align: center;"> $27 - j15$ $3 - 25 + j5$ </p> <p style="text-align: right;"> $-25 + j5$ $27 - 5j$ </p>		

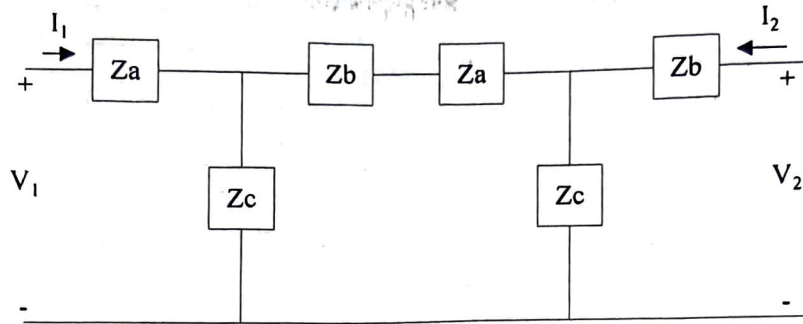

UNIT-IV

12

Design m-derived T-sections HPFs for $R_0 = 600$ ohms, $f_c = 1800$ Hz and $f_\infty = 2000$ Hz. **10**

13

An impedance is given by $Z(s) = \frac{3s^2 + 18s + 24}{s^2 + 3s}$. Realize the network in Foster-I form. **10**

$$3 \left(s^2 + 6s \right)$$